

Report

GROUP: 5

(SEC1: {Ahmed Mohammed AbdelFattah (25)-Ahmed Mohammed Fawzy (26)-Ahmed Morsy Abbas (29)-Ahmed Hendaway Maher (32)-Adham Mohammed Eid (34)-Eslam Khaled Kamal (37)})

SEC3 :{ Abdullah Hashem Rashad (2)}

RFID Attendance Project

Overview:

This circuit is simply a counter for attendance of lectures, where each student has an assigned card that he uses on entrance to the lecture.

Features:

The project has some basic abilities as:

- 1- A button that display the number of attendance and absent students.
- 2- A button that display the names of present students.

Also some characteristics as:

- 1- A timer to stop taking attendance as wanted (ex: after 30 minutes no allowed students to enter).

Future modifications:

The actions taken after registration of a card can vary as:

- 1-It can be made to control the door of the lecture hall.
- 2-A keypad can be added to the circuit, where no attendance can be taken before a specified password entered by the management.

Explanation:

The circuit works as an embedded system where a code is used to be burned on a microcontroller to carry out the desired procedures.

In this project we used an ATMEGA32 microcontroller programmed by the AVR studio to work as the system we wanted.

Components:


- 1- ATMEGA32 microcontroller.
- 2- LCD (16*2).
- 3- RFID module.
- 4- RFID sensor (coil).
- 5- IC 555 (timer).
- 6- Resistances.
- 7- LEDs.
- 8- Capacitors.
- 9- Buttons.
- 10- Crystal capacitor.
- 11- A power supply.

Timer circuit:

This circuit was made by an IC 555, a resistance and a capacitor.

The delay time given by the circuit depends on the value of the resistance and the capacitor, where

$$\text{Delay time} = \ln(3) * R * C.$$

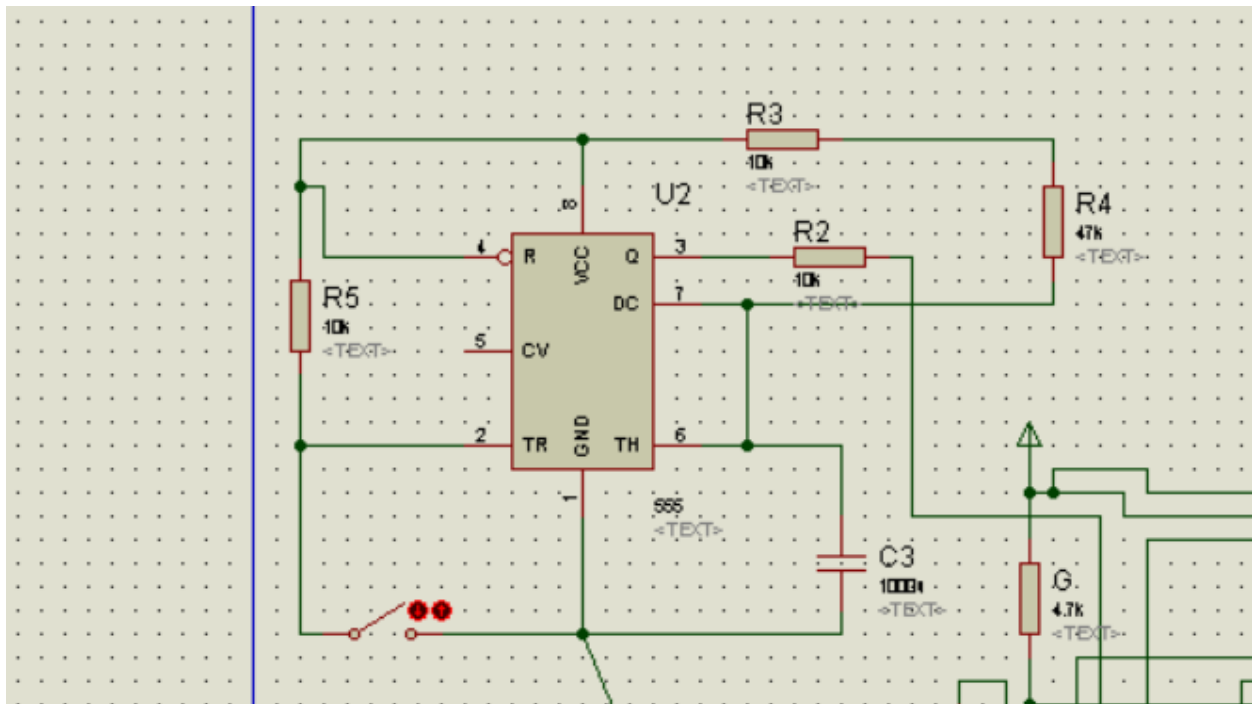

Procedure:

When the button of the timer is pushed it start to count and the code starts to run and the RFID cards can start to be registered.

As a card is run the name of the student is displayed, and if a wrong one is registered a red led flashes and a message “Wrong ID” appears on the screen.

At wish, the buttons can be used:

- 1- switch 1 :(display list of present students).
- 2- switch 2 :(displays number of present and absent students).

After the time of timer set to count the code is stopped and no more cards are allowed to enter.

switch 3: (timer button)


Instruction:


To make it works, do as follows:

- 1- Close switch 3 then open it.
- 2- Open virtual terminal ,and start registering the ID cards
(2014,2015,2016,2017,2018,2018,2019,2020)(any other code is invalid)
- 3- Wait for one minute and the circuit will not accept any code again.
- 4- Then you can use one of the switches (switch 1or switch 2).
- 5- That's all THANK YOU.


Simulation:

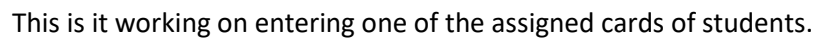This is the simulation of the hardware of the circuit.



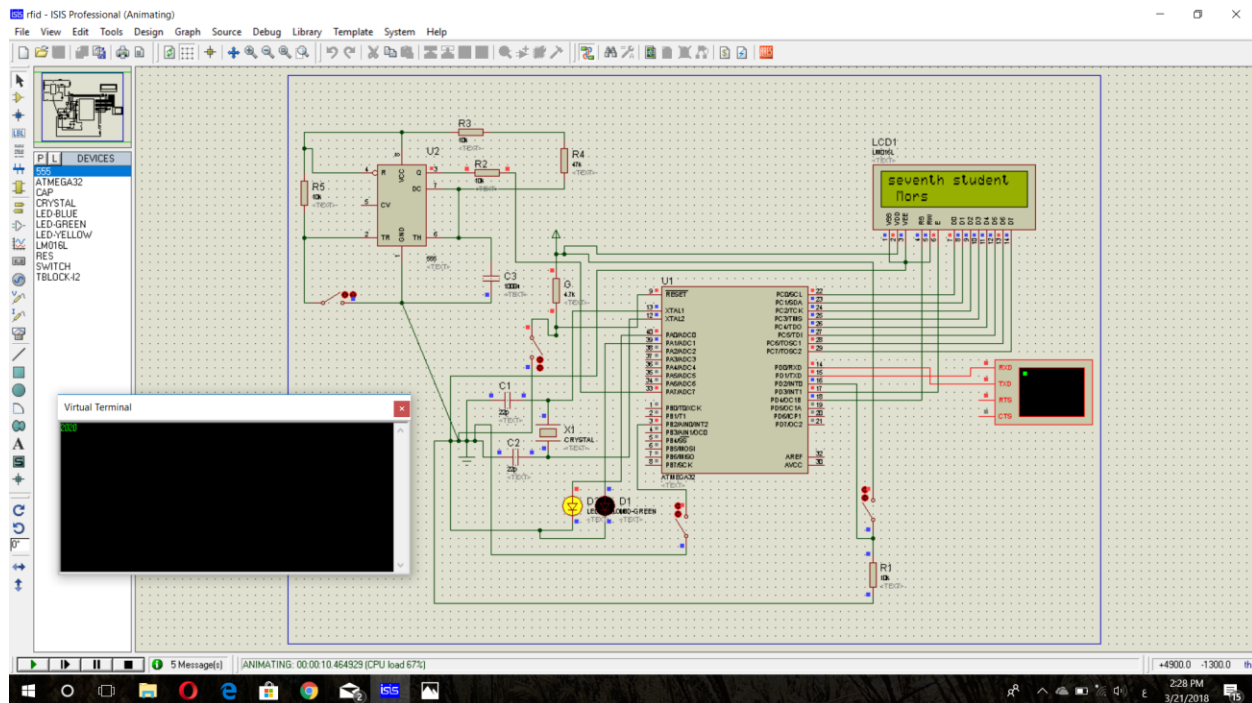


This when an invalid card id entered.

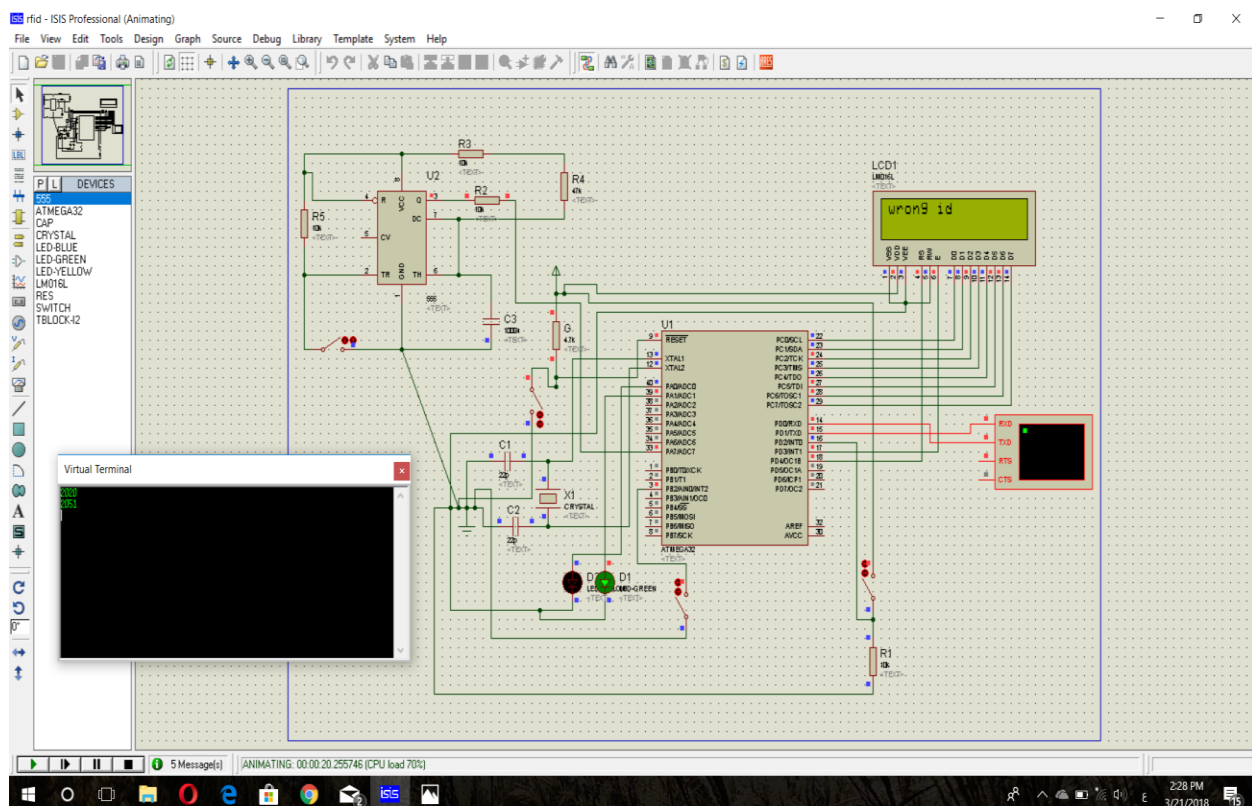


This when display button 2 is pressed:

Absent number.

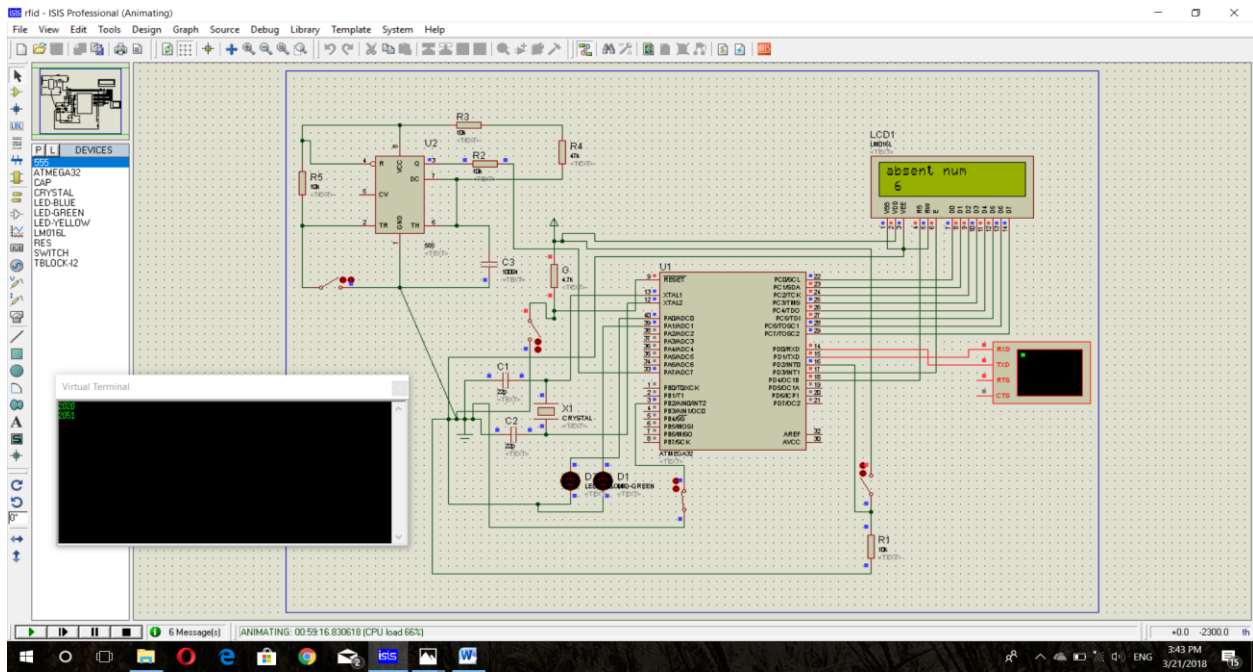


Present number

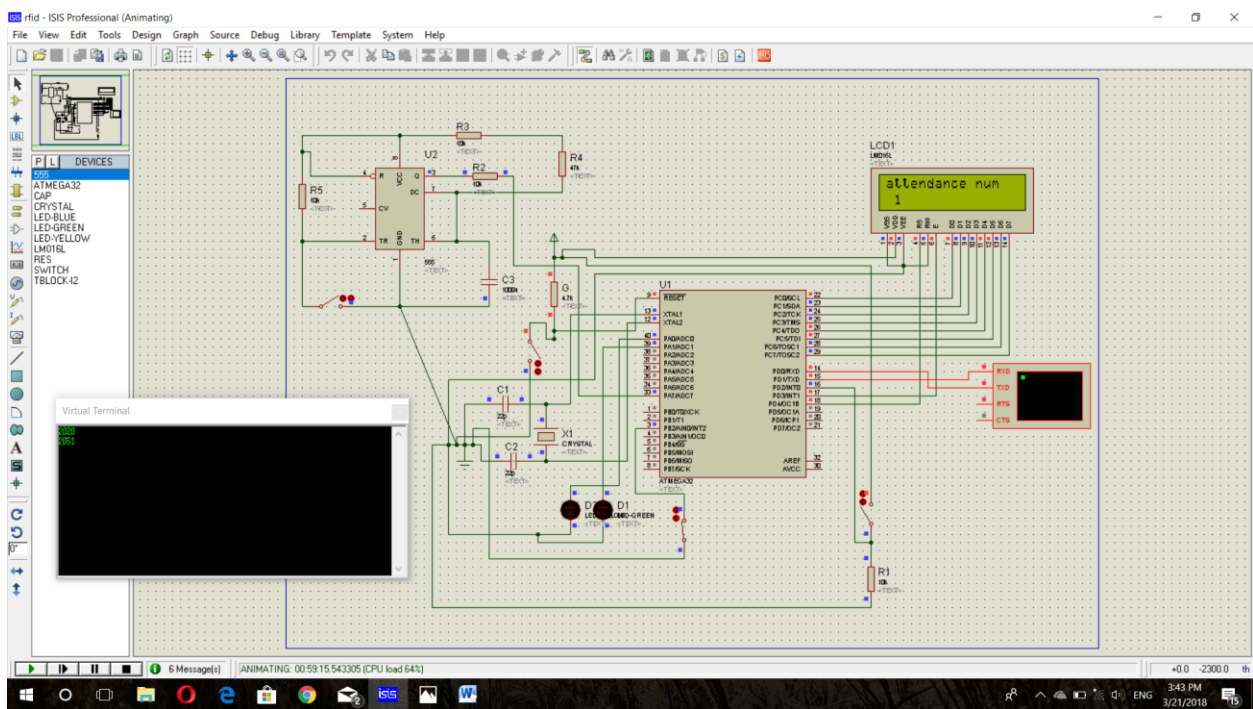



Displaying list of present students

(Ex. only one present)

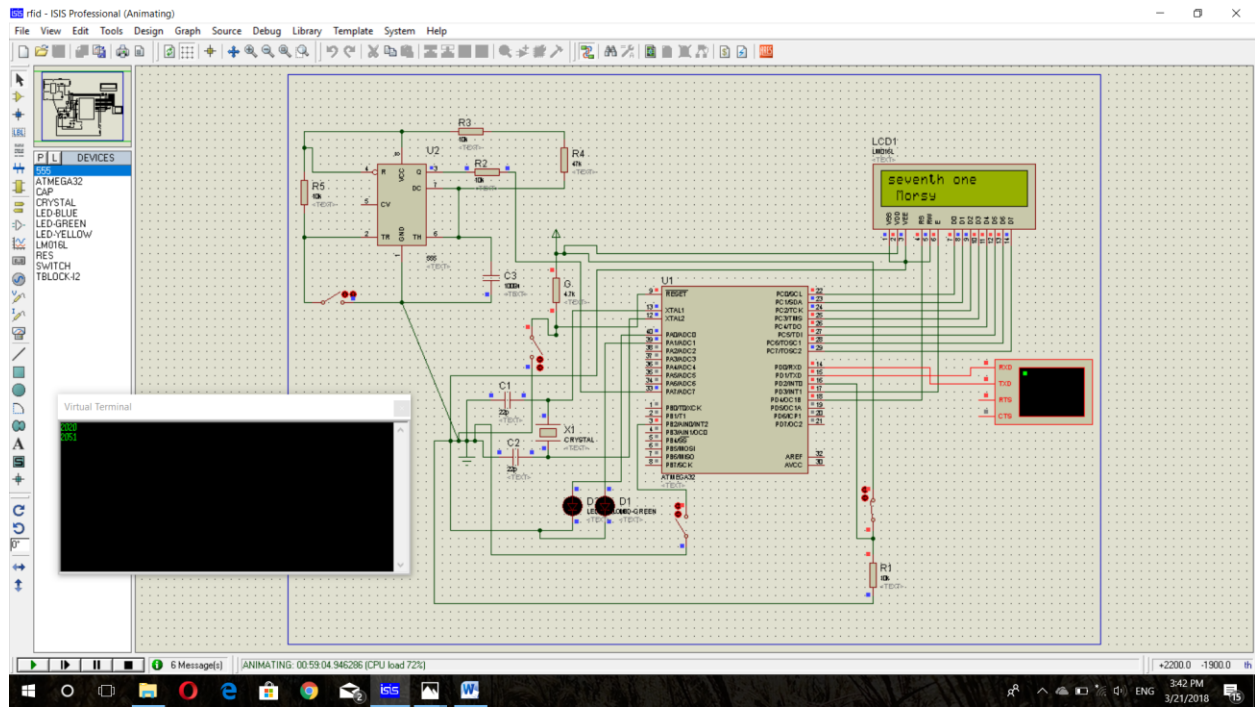

PCB Design:

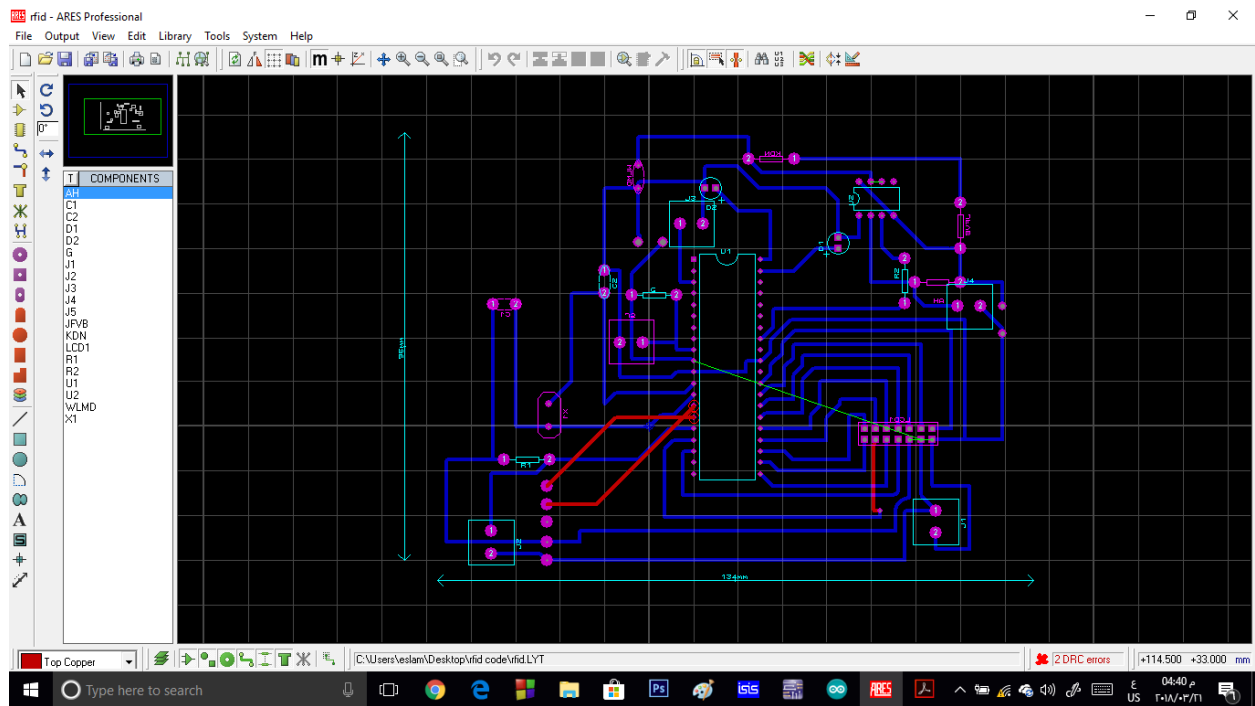

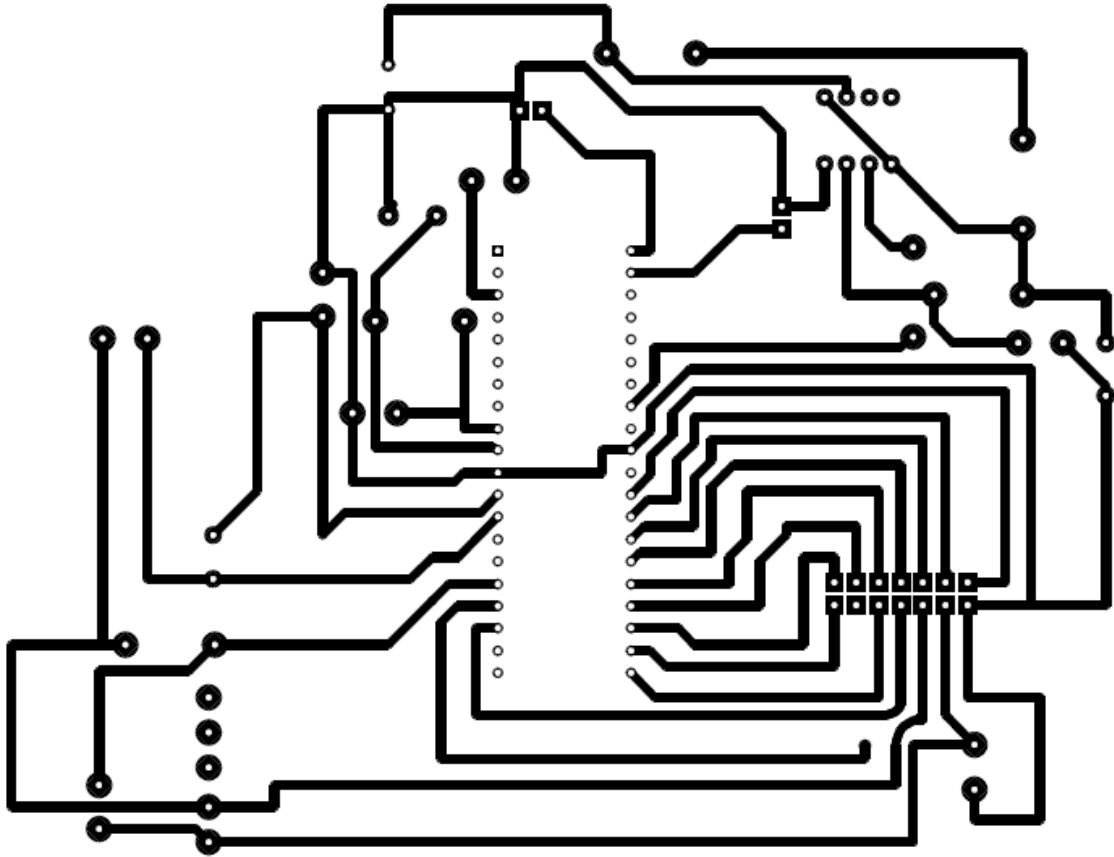

Programs used:

- 1- Proteus (ISIS –ARES).
- 2- Atmel studio.
- 3- Microsoft word.